

# Lab 9-10 – Nanoprocessor Design Competition

CS1050 Computer Organization and Digital Design  
Dept. of Computer Science and Engineering  
University of Moratuwa

## Group members

- Name :- Sampath W.I.D  
Reg. No :- 230571F
- Name :- Dabarera G.D.M  
Reg. No :- 230111X
- Name :- Kannangara T.P  
Reg. No :- 230315C
- Name :- Priyadarshana D.M.R.N  
Reg. No :- 230501T

## Lab Task

1. **Execute Simple Programs Using a 4-bit Processor**  
The primary goal is to run simple programs and obtain results using a custom-designed 4-bit processor capable of executing 8 basic instructions.
2. **Develop a 4-bit Arithmetic Unit**  
A core component of the processor is a 4-bit arithmetic unit designed to perform both addition and subtraction on signed integers efficiently.
3. **Implement Instruction Decoding**  
To correctly execute instructions, an Instruction Decoder is developed to activate the appropriate internal components of the processor based on the input operation.
4. **Design Multiplexers or Tri-State Buses**  
k-way, b-bit multiplexers and/or tri-state buses are designed to manage data flow and control signal selection throughout the processor architecture.
5. **Simulate and Test for Verification**  
Once design and development are completed, all components are thoroughly tested through simulations and validated on a development board to ensure proper functionality.
6. **Practice Effective Team Collaboration**  
Team members enhance their skills in communication, task sharing, coordination, and integration of separately developed modules to form a cohesive system.

## VHDL Files

## 4-bit Add/Sub Unit

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Add_Sub_4bit is
    Port ( A : in STD_LOGIC_VECTOR(3 downto 0);
          B : in STD_LOGIC_VECTOR(3 downto 0);
          AddSubSelect : in STD_LOGIC;
          S : inout STD_LOGIC_VECTOR(3 downto 0);
          Zero : out STD_LOGIC;
          Overflow : out STD_LOGIC);
end Add_Sub_4bit;

architecture Behavioral of Add_Sub_4bit is
    component FA
        port(
            A: in std_logic;
            B: in std_logic;
            C_in: in std_logic;
            S: out std_logic;
            C_out: out std_logic);
    end component;

    signal FA0_C, FA1_C, FA2_C : STD_LOGIC;
    signal B0_xor, B1_xor, B2_xor, B3_xor : STD_LOGIC;

begin
    B0_xor <= B(0) xor AddSubSelect;
    B1_xor <= B(1) xor AddSubSelect;
    B2_xor <= B(2) xor AddSubSelect;
    B3_xor <= B(3) xor AddSubSelect;
    FA_0: FA
        port map(
            A => A(0),
            B => B0_xor,
            C_in => AddSubSelect,
            S => S(0),
            C_out => FA0_C);

    FA_1: FA
        port map(

```

```

    A => A(1),
    B => B1_xor,
    C_in => FA0_C,
    S => S(1),
    C_out => FA1_C);

FA_2: FA
port map(
    A => A(2),
    B => B2_xor,
    C_in => FA1_C,
    S => S(2),
    C_out => FA2_C);

FA_3: FA
port map(
    A => A(3),
    B => B3_xor,
    C_in => FA2_C,
    S => S(3),
    C_out => Overflow);

Zero <= NOT(S(0) OR S(1) OR S(2) OR S(3));

end Behavioral;

```

### 3-bit Program Counter

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity PC_3bit is
    Port (
        Reset      : in  STD_LOGIC;
        Clk        : in  STD_LOGIC;
        MemorySelect : out STD_LOGIC_VECTOR(2 downto 0);
        JumpAddr    : in  STD_LOGIC_VECTOR(2 downto 0);
        JumpFlag    : in  STD_LOGIC
    );
end PC_3bit;

architecture Behavioral of PC_3bit is
    signal PC_reg : std_logic_vector(2 downto 0) := "000";

```

```

begin
  process(Clk, Reset)
  begin
    if Reset = '1' then
      PC_reg <= "000";
    elsif rising_edge(Clk) then
      if JumpFlag = '1' then
        PC_reg <= JumpAddr;
      else
        case PC_reg is
          when "000" => PC_reg <= "001";
          when "001" => PC_reg <= "010";
          when "010" => PC_reg <= "011";
          when "011" => PC_reg <= "100";
          when "100" => PC_reg <= "101";
          when "101" => PC_reg <= "110";
          when "110" => PC_reg <= "111";
          when others => PC_reg <= "000";
        end case;
      end if;
    end if;
  end process;

  MemorySelect <= PC_reg;
end Behavioral;

```

#### Program Rom

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

entity Program_ROM is
  Port ( MemSelect : in STD_LOGIC_VECTOR (2 downto 0);
        InstructBus : out STD_LOGIC_VECTOR (11 downto 0));
end Program_ROM;

architecture Behavioral of Program_ROM is

  type rom_type is array (0 to 7) of std_logic_vector(11 downto 0);

  signal Assembly_Code : rom_type := (
    "101110000000", -- 0
    "100010000001", -- 1
    "100100000010", -- 2

```

```

        "100110000011", -- 3
        "001110010000", -- 4
        "001110100000", -- 5
        "001110110000", -- 6
        "110000000111"  -- 7
    );
begin
    InstructBus <= Assembly_Code(to_integer(unsigned(MemSelect)));
end Behavioral;

```

### Register Bank

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Register_Bank is
    Port ( D_input : in STD_LOGIC_VECTOR (3 downto 0);
          Reg_En : in STD_LOGIC_VECTOR (2 downto 0);
          Clock : in STD_LOGIC;
          Reset : in STD_LOGIC;
          D_out0 : out STD_LOGIC_VECTOR (3 downto 0) := "0000";
          D_out1 : out STD_LOGIC_VECTOR (3 downto 0);
          D_out2 : out STD_LOGIC_VECTOR (3 downto 0);
          D_out3 : out STD_LOGIC_VECTOR (3 downto 0);
          D_out4 : out STD_LOGIC_VECTOR (3 downto 0);
          D_out5 : out STD_LOGIC_VECTOR (3 downto 0);
          D_out6 : out STD_LOGIC_VECTOR (3 downto 0);
          D_out7 : out STD_LOGIC_VECTOR (3 downto 0));
end Register_Bank;

```

architecture Behavioral of Register\_Bank is

```

    component Decoder_3_to_8 is
        Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
              EN : in STD_LOGIC;
              Y : out STD_LOGIC_VECTOR (7 downto 0));
    end component;

```

```

    component Reg is
        Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
              En : in STD_LOGIC;
              Clk : in STD_LOGIC;
              Reset : in STD_LOGIC;
              Q : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

```

```
end component;

signal y : STD_LOGIC_VECTOR (7 downto 0);

begin
    decoder : Decoder_3_to_8
    port map (
        I => Reg_En,
        En => '1',
        Y => y );

    Reg0 : Reg
    port map (
        D => D_input,
        En => '0',
        Clk => Clock,
        Reset => Reset,
        Q => D_out0 );

    Reg1 : Reg
    port map (
        D => D_input,
        En => y(1),
        Clk => Clock,
        Reset => Reset,
        Q => D_out1 );

    Reg2 : Reg
    port map (
        D => D_input,
        En => y(2),
        Clk => Clock,
        Reset => Reset,
        Q => D_out2 );

    Reg3 : Reg
    port map (
        D => D_input,
        En => y(3),
        Clk => Clock,
        Reset => Reset,
        Q => D_out3 );

    Reg4 : Reg
    port map (
        D => D_input,
```

```

    En => y(4),
    Clk => Clock,
    Reset => Reset,
    Q => D_out4 );

```

```

Reg5 : Reg
port map (
    D => D_input,
    En => y(5),
    Clk => Clock,
    Reset => Reset,
    Q => D_out5 );

```

```

Reg6 : Reg
port map (
    D => D_input,
    En => y(6),
    Clk => Clock,
    Reset => Reset,
    Q => D_out6 );

```

```

Reg7 : Reg
port map (
    D => D_input,
    En => y(7),
    Clk => Clock,
    Reset => Reset,
    Q => D_out7 );

```

```

end Behavioral;

```

## Register

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Reg is
    Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
          En : in STD_LOGIC;
          Clk : in STD_LOGIC;
          Reset : in STD_LOGIC;    -- add reset pin for reset
    output
        Q : out STD_LOGIC_VECTOR (3 downto 0));
end Reg;

```

architecture Behavioral of Reg is

```
begin
    process(Clk) begin
        if (Reset = '1') then
            Q <= (others => '0');
        elsif (rising_edge(Clk)) then
            if En = '1' then
                Q <= D;
            end if;
        end if;
    end process;

end Behavioral;
```

## Counter

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Counter is
    Port ( Dir : in STD_LOGIC;
          Res : in STD_LOGIC;
          Clk : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (2 downto 0));
end Counter;
```

architecture Behavioral of Counter is

```
COMPONENT D_FF
PORT (
    D : in STD_LOGIC;
    Res : in STD_LOGIC;
    Clk : in STD_LOGIC;
    Q : out STD_LOGIC;
    Qbar : out STD_LOGIC );
END COMPONENT;

COMPONENT Slow_Clk
PORT (
    Clk_in : in STD_LOGIC;
    Clk_out : out STD_LOGIC );
END COMPONENT;
```



```
signal D0, D1, D2 : std_logic;
signal Q0, Q1, Q2 : std_logic;
signal Clk_slow : std_logic;

begin

    Slow_Clk0 : Slow_Clk
        port map (
            Clk_in => Clk,
            Clk_out => Clk_slow );

    D0 <= ((not Q2) and (not Dir)) or (Q1 and Dir);
    D1 <= (Q0 and (not Dir)) or (Q2 and Dir);
    D2 <= (Q1 and (not Dir)) or ((not Q0) and Dir);

    D_FF0 : D_FF
        port map (
            D => D0,
            Res => Res,
            Clk => Clk_Slow,
            Q => Q0 );

    D_FF1 : D_FF
        port map (
            D => D1,
            Res => Res,
            Clk => Clk_Slow,
            Q => Q1 );

    D_FF2 : D_FF
        port map (
            D => D2,
            Res => Res,
            Clk => Clk_Slow,
            Q => Q2 );

    Q(0) <= Q0;
    Q(1) <= Q1;
    Q(2) <= Q2;

end Behavioral;
```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Decoder_3_to_8 is
    Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
          EN : in STD_LOGIC;
          Y : out STD_LOGIC_VECTOR (7 downto 0));
end Decoder_3_to_8;

architecture Behavioral of Decoder_3_to_8 is
    component Decoder_2_to_4 port(
        I: in STD_LOGIC_VECTOR;
        EN: in STD_LOGIC;
        Y: out STD_LOGIC_VECTOR );
    end component;
    signal I0,I1 : STD_LOGIC_VECTOR(1 downto 0);
    signal Y0,Y1 : STD_LOGIC_VECTOR (3 downto 0);
    signal en0,en1, I2 : STD_LOGIC;

begin
    Decode_2_to_4_0 : Decoder_2_to_4
    port map(
        I => I0,
        EN => en0,
        Y => Y0 );

    Decode_2_to_4_1 : Decoder_2_to_4
    port map(
        I => I1,
        EN => en1,
        Y => Y1 );

    en0 <= NOT(I(2)) AND EN;
    en1 <= I(2) AND EN;
    I0 <= I(1 downto 0);
    I1 <= I(1 downto 0);
    I2 <= I(2);
    Y(3 downto 0) <= Y0;
    Y(7 downto 4) <= Y1;

end Behavioral;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

entity LUT_16_7 is
    Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
          data : out STD_LOGIC_VECTOR (6 downto 0));
end LUT_16_7;

architecture Behavioral of LUT_16_7 is

    type rom_type is array (0 to 15) of std_logic_vector(6 downto 0);
    signal sevenSegment_ROM : rom_type := (
        "1000000", -- 0      0= on 1=off    g f e d c b a
        "1111001", -- 1
        "0100100", -- 2
        "0110000", -- 3
        "0011001", -- 4
        "0010010", -- 5
        "0000010", -- 6
        "1111000", -- 7
        "0000000", -- 8
        "0010000", -- 9
        "0001000", -- a
        "0000011", -- b
        "1000110", -- c
        "0100001", -- d
        "0000110", -- e
        "0001110"  -- f
    );

begin
    data <= sevenSegment_ROM(to_integer(unsigned(address)));

end Behavioral;

```

#### Slow Clock

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Slow_Clk is
    Port ( Clk_in : in STD_LOGIC;
          Clk_out : out STD_LOGIC);
end Slow_Clk;

```

architecture Behavioral of Slow\_Clk is

```

signal count : integer := 1;
signal clk_status : std_logic := '0';

begin
    process (Clk_in) begin
        if (rising_edge(Clk_in)) then
            count <= count + 1;
            if(count = 5) then --50000000 for project (5 for test)
                clk_status <= not clk_status;
                Clk_out <= clk_status;
                count <= 1;
            end if;
        end if;
    end process;

end Behavioral;
```

#### MUX 2way 4bit

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux_2way_4bit is
    Port ( AddSub : in STD_LOGIC_VECTOR (3 downto 0);
          Immediate_Val : in STD_LOGIC_VECTOR (3 downto 0);
          Load_Select : in STD_LOGIC;
          output : out STD_LOGIC_VECTOR (3 downto 0));
end Mux_2way_4bit;

architecture Behavioral of Mux_2way_4bit is

    COMPONENT Mux_2_to_1
    PORT ( D : in STD_LOGIC_VECTOR (1 downto 0);
          S : in STD_LOGIC;
          Y : out STD_LOGIC);
    END COMPONENT;

begin
    Mux_0: Mux_2_to_1 port map(
        D(1) => AddSub(0),
        D(0) => Immediate_Val(0),
        S => Load_Select,
```

```

        Y => output(0)
    );

    Mux_1: Mux_2_to_1 port map(
        D(1) => AddSub(1),
        D(0) => Immediate_Val(1),
        S => Load_Select,
        Y => output(1)
    );

    Mux_2: Mux_2_to_1 port map(
        D(1) => AddSub(2),
        D(0) => Immediate_Val(2),
        S => Load_Select,
        Y => output(2)
    );

    Mux_3: Mux_2_to_1 port map(
        D(1) => AddSub(3),
        D(0) => Immediate_Val(3),
        S => Load_Select,
        Y => output(3)
    );

end Behavioral;

```

#### MUX 2way 3bit

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux_2way_3bit is
    Port ( jmp_adrs : in STD_LOGIC_VECTOR (2 downto 0);
          adder_3bit : in STD_LOGIC_VECTOR (2 downto 0);
          jmp_flag : in STD_LOGIC;
          output : out STD_LOGIC_VECTOR (2 downto 0));
end Mux_2way_3bit;

architecture Behavioral of Mux_2way_3bit is
    COMPONENT Mux_2_to_1
        PORT ( D : in STD_LOGIC_VECTOR (1 downto 0);
              S : in STD_LOGIC;
              Y : out STD_LOGIC);
    END COMPONENT;

begin

```

```

Mux_0: Mux_2_to_1 port map(
    D(0) => jmp_adrs(0),
    D(1) => adder_3bit(0),
    S => jmp_flag,
    Y => output(0)
);

Mux_1: Mux_2_to_1 port map(
    D(0) => jmp_adrs(1),
    D(1) => adder_3bit(1),
    S => jmp_flag,
    Y => output(1)
);

Mux_2: Mux_2_to_1 port map(
    D(0) => jmp_adrs(2),
    D(1) => adder_3bit(2),
    S => jmp_flag,
    Y => output(2)
);

```

end Behavioral;

#### MUX 8way 4bit

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux_8way_4bit is
    Port (
        reg0 : in STD_LOGIC_VECTOR (3 downto 0);
        reg1 : in STD_LOGIC_VECTOR (3 downto 0);
        reg2 : in STD_LOGIC_VECTOR (3 downto 0);
        reg3 : in STD_LOGIC_VECTOR (3 downto 0);
        reg4 : in STD_LOGIC_VECTOR (3 downto 0);
        reg5 : in STD_LOGIC_VECTOR (3 downto 0);
        reg6 : in STD_LOGIC_VECTOR (3 downto 0);
        reg7 : in STD_LOGIC_VECTOR (3 downto 0);
        Reg_select : in STD_LOGIC_VECTOR (2 downto 0);
        output : out STD_LOGIC_VECTOR (3 downto 0));
end Mux_8way_4bit;

architecture Behavioral of Mux_8way_4bit is

begin

```

```

    process(reg0, reg1, reg2, reg3, reg4, reg5, reg6, reg7,
Reg_select)
    begin
        case (Reg_select) is
            when "000" =>
                output <= reg0;
            when "001" =>
                output <= reg1;
            when "010" =>
                output <= reg2;
            when "011" =>
                output <= reg3;
            when "100" =>
                output <= reg4;
            when "101" =>
                output <= reg5;
            when "110" =>
                output <= reg6;
            when "111" =>
                output <= reg7;
            when others =>
                output <= "0000"; -- For handle any undefined
        cases
            end case;
        end process;
    end Behavioral;

```

#### Instruction Decoder

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Instruction_Dec is
    Port ( Reg_En : out STD_LOGIC_VECTOR (2 downto 0);
          Load_Select : out STD_LOGIC;
          Immediate_Val : out STD_LOGIC_VECTOR (3 downto 0);
          MuxA_Select : out STD_LOGIC_VECTOR (2 downto 0);
          MuxB_Select : out STD_LOGIC_VECTOR (2 downto 0);
          AddSub_Select : out STD_LOGIC;
          JmpFlag : out STD_LOGIC;
          JmpAddr : out STD_LOGIC_VECTOR (2 downto 0);
          Instruct_Bus : in STD_LOGIC_VECTOR (11 downto 0);
          JumpCheck : in STD_LOGIC_VECTOR (3 downto 0));
end Instruction_Dec;

```

architecture Behavioral of Instruction\_Dec is

```

begin
  process(Instruct_Bus, JumpCheck)
  begin

    -- for ADD intruction
    if Instruct_Bus (11 downto 10) = "00" then
      JmpFlag <= '0';

      MuxA_Select <= Instruct_Bus (9 downto 7);
      MuxB_Select <= Instruct_Bus (6 downto 4);
      AddSub_Select <= '0';
      Load_Select <= '0';
      Reg_En <= Instruct_Bus (9 downto 7); -- Store the
result on Register A

      -- for NEG intruction
      elsif Instruct_Bus (11 downto 10) = "01" then
        JmpFlag <= '0';

        MuxA_Select <= "000"; -- For get -B we have to set A
to zero(i.e. set to Register 0) because adder perform only A+B.
        MuxB_Select <= Instruct_Bus (9 downto 7); -- For get a
negative value of a particular number, it can be only done from
Mux B
        AddSub_Select <= '1'; -- Here we perform only
subtraction.
        Load_Select <= '0';
        Reg_En <= Instruct_Bus (9 downto 7); -- Store the
result on Register A

        -- for MOV intruction
        elsif Instruct_Bus (11 downto 10) = "10" then
          JmpFlag <= '0';
          MuxA_Select <= "000";
          MuxB_Select <= "000";

          Immediate_Val <= Instruct_Bus (3 downto 0);
          Reg_En <= Instruct_Bus (9 downto 7);
          Load_Select <= '1'; -- Select IMMEDIATE VALUE port via

        -- for JMP intruction
        else
          MuxB_Select <= "000";
          Immediate_Val <= "0000";
          Load_Select <= '1';

```



```

    Reg_En <= "000";

    MuxA_Select <= Instruct_Bus (9 downto 7);
    if JumpCheck = "0000" then
        JmpAddr <= Instruct_Bus (2 downto 0);
        JmpFlag <= '1';
    else
        JmpFlag <= '0';
    end if;
end if;
end process;

end Behavioral;

```

### Nano Processor

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Nanoprocessor is
    Port ( Reset : in STD_LOGIC;
          clk : in STD_LOGIC;
          Zero_LED : out STD_LOGIC := '1';
          Overflow_LED : out STD_LOGIC;
          LED0 : out STD_LOGIC;
          LED1 : out STD_LOGIC;
          LED2 : out STD_LOGIC;
          LED3 : out STD_LOGIC;
          Anode : out STD_LOGIC_VECTOR (3 downto 0);
          S_7Seg : out STD_LOGIC_VECTOR (6 downto 0)
    );
end Nanoprocessor;

architecture Behavioral of Nanoprocessor is

    component Register_Bank is
        Port ( D_input : in STD_LOGIC_VECTOR (3 downto 0);
              Reg_En : in STD_LOGIC_VECTOR (2 downto 0);
              Clock : in STD_LOGIC;
              Reset : in STD_LOGIC;
              D_out0 : out STD_LOGIC_VECTOR (3 downto 0);
              D_out1 : out STD_LOGIC_VECTOR (3 downto 0);
              D_out2 : out STD_LOGIC_VECTOR (3 downto 0);
              D_out3 : out STD_LOGIC_VECTOR (3 downto 0);
              D_out4 : out STD_LOGIC_VECTOR (3 downto 0);
              D_out5 : out STD_LOGIC_VECTOR (3 downto 0);

```

```

        D_out6 : out STD_LOGIC_VECTOR (3 downto 0);
        D_out7 : out STD_LOGIC_VECTOR (3 downto 0));
end component;

```

```

component Mux_8way_4bit is

```

```

    Port (  reg0 : in STD_LOGIC_VECTOR (3 downto 0);
            reg1 : in STD_LOGIC_VECTOR (3 downto 0);
            reg2 : in STD_LOGIC_VECTOR (3 downto 0);
            reg3 : in STD_LOGIC_VECTOR (3 downto 0);
            reg4 : in STD_LOGIC_VECTOR (3 downto 0);
            reg5 : in STD_LOGIC_VECTOR (3 downto 0);
            reg6 : in STD_LOGIC_VECTOR (3 downto 0);
            reg7 : in STD_LOGIC_VECTOR (3 downto 0);
            Reg_select : in STD_LOGIC_VECTOR (2 downto 0);
            output : out STD_LOGIC_VECTOR (3 downto 0));

```

```

end component;

```

```

component Add_Sub_4bit is

```

```

    Port (
        A : in STD_LOGIC_VECTOR(3 downto 0);
        B : in STD_LOGIC_VECTOR(3 downto 0);
        AddSubSelect : in STD_LOGIC;
        S : inout STD_LOGIC_VECTOR(3 downto 0);
        Zero : out STD_LOGIC;
        Overflow : out STD_LOGIC
    );

```

```

end component;

```

```

component Instruction_Dec is

```

```

    Port ( Reg_En : out STD_LOGIC_VECTOR (2 downto 0);
            Load_Select : out STD_LOGIC;
            Immediate_Val : out STD_LOGIC_VECTOR (3 downto 0);
            MuxA_Select : out STD_LOGIC_VECTOR (2 downto 0);
            MuxB_Select : out STD_LOGIC_VECTOR (2 downto 0);
            AddSub_Select : out STD_LOGIC;
            JmpFlag : out STD_LOGIC;
            JmpAddr : out STD_LOGIC_VECTOR (2 downto 0);
            Instruct_Bus : in STD_LOGIC_VECTOR (11 downto 0);
            JumpCheck : in STD_LOGIC_VECTOR (3 downto 0));

```

```

end component;

```

```

component Program_ROM is

```

```

    Port ( MemSelect : in STD_LOGIC_VECTOR (2 downto 0);
            InstructBus : out STD_LOGIC_VECTOR (11 downto 0));

```

```

end component;

```

```

component PC_3bit is
    Port ( Reset : in STD_LOGIC;
          Clk : in STD_LOGIC;
          MemorySelect : inout STD_LOGIC_VECTOR (2 downto 0);
          JumpAddr : in STD_LOGIC_VECTOR (2 downto 0);
-- If there is a jump instruction, PC set MemorySelect as the
          JumpFlag : in STD_LOGIC);
end component;

component Mux_2way_4bit is
    Port ( AddSub : in STD_LOGIC_VECTOR (3 downto 0);
          Immediate_Val : in STD_LOGIC_VECTOR (3 downto 0);
          Load_Select : in STD_LOGIC;
          output : out STD_LOGIC_VECTOR (3 downto 0));
end component;

component Slow_Clk
    Port ( Clk_in : in STD_LOGIC;
          Clk_out : out STD_LOGIC );
end component;

component LUT_16_7 is
    Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
          data : out STD_LOGIC_VECTOR (6 downto 0));
end component;

signal Clk_slow : std_logic;
signal Memory_Select : std_logic_vector (2 downto 0); -- from
program counter to program ROM
signal Jump_Address : std_logic_vector (2 downto 0); -- from
instruction decoder to program counter
signal Jump_Flag : std_logic; -- from instruction decoder to
program counter
signal I : std_logic_vector (11 downto 0); -- from program ROM to
instruction decoder
signal Register_Enable : std_logic_vector (2 downto 0); -- from
instruction decoder to Register Bank
signal Load_Select : std_logic; -- from instruction decoder to
Mux_2way_4bit
signal Immediate_Value : std_logic_vector (3 downto 0); -- from
instruction decoder to Mux_2way_4bit
signal Mux_A_Select : std_logic_vector (2 downto 0); -- from
instruction decoder to Mux_8way_4bit(A)
signal Mux_B_Select : std_logic_vector (2 downto 0); -- from
instruction decoder to Mux_8way_4bit(B)

```

```

signal ADD_SUB_Select : std_logic; -- from instruction decoder to
Add_Sub_4bit
signal Mux_A : std_logic_vector (3 downto 0); -- from
Mux_8way_4bit(A) to Add_Sub_4bit / from instruction decoder to
Mux_8way_4bit(A) output
signal Mux_B : std_logic_vector (3 downto 0); -- from
Mux_8way_4bit(B) to Add_Sub_4bit
signal Add_Sub_Result : std_logic_vector (3 downto 0); -- from
Add_Sub_4bit to Mux_2way_4bit
signal Register_Input : std_logic_vector (3 downto 0); -- from
Mux_2way_4bit to Register Bank
signal R0 : std_logic_vector (3 downto 0); -- from R0 to
Mux_8way_4bit
signal R1 : std_logic_vector (3 downto 0); -- from R1 to
Mux_8way_4bit
signal R2 : std_logic_vector (3 downto 0); -- from R2 to
Mux_8way_4bit
signal R3 : std_logic_vector (3 downto 0); -- from R3 to
Mux_8way_4bit
signal R4 : std_logic_vector (3 downto 0); -- from R4 to
Mux_8way_4bit
signal R5 : std_logic_vector (3 downto 0); -- from R5 to
Mux_8way_4bit
signal R6 : std_logic_vector (3 downto 0); -- from R6 to
Mux_8way_4bit
signal R7 : std_logic_vector (3 downto 0); -- from R7 to
Mux_8way_4bit

```

```

signal S_7s : STD_LOGIC_VECTOR (6 downto 0) := "0000000";
--signal clk_7seg : STD_LOGIC;

```

```

begin

```

```

Slow_Clock : Slow_Clk
port map (
    Clk_in => clk,
    Clk_out => Clk_slow
);

```

```

LUT_16_7_0 : LUT_16_7
port map (
    address => R7,
    data => S_7s
);

```

```
Programming_Counter : PC_3bit
port map (
    Reset => Reset,
    Clk => Clk_slow,
    MemorySelect => Memory_Select,
    JumpAddr => Jump_Address,
    JumpFlag => Jump_Flag
);

Program_ROM0 : Program_ROM
port map (
    MemSelect => Memory_Select,
    InstructBus => I
);

Instruction_Decoder : Instruction_Dec
port map (
    Reg_En => Register_Enable,
    Load_Select => Load_Select,
    Immediate_Val => Immediate_Value,
    MuxA_Select => Mux_A_Select,
    MuxB_Select => Mux_B_Select,
    AddSub_Select => ADD_SUB_Select,
    JmpFlag => Jump_Flag,
    JmpAddr => Jump_Address,
    Instruct_Bus => I,
    JumpCheck => Mux_A
);

Mux_2way_4bit0 : Mux_2way_4bit
port map (
    AddSub => Add_Sub_Result,
    Immediate_Val => Immediate_Value,
    Load_Select => Load_Select,
    output => Register_Input
);

Add_Sub_Unit : Add_Sub_4bit
port map (
    A => Mux_A,
    B => Mux_B,
    AddSubSelect => ADD_SUB_Select,
    S => Add_Sub_Result,
    Zero => Zero_LED,
    Overflow => Overflow_LED
);
```

```
);
```

```
MuxA : Mux_8way_4bit
```

```
port map (
```

```
    reg0 => R0,
```

```
    reg1 => R1,
```

```
    reg2 => R2,
```

```
    reg3 => R3,
```

```
    reg4 => R4,
```

```
    reg5 => R5,
```

```
    reg6 => R6,
```

```
    reg7 => R7,
```

```
    Reg_select => Mux_A_Select,
```

```
    output => Mux_A
```

```
);
```

```
MuxB : Mux_8way_4bit
```

```
port map (
```

```
    reg0 => R0,
```

```
    reg1 => R1,
```

```
    reg2 => R2,
```

```
    reg3 => R3,
```

```
    reg4 => R4,
```

```
    reg5 => R5,
```

```
    reg6 => R6,
```

```
    reg7 => R7,
```

```
    Reg_select => Mux_B_Select,
```

```
    output => Mux_B
```

```
);
```

```
RegisterBank : Register_Bank
```

```
port map (
```

```
    D_input => Register_Input,
```

```
    Reg_En => Register_Enable,
```

```
    Clock => Clk_slow,
```

```
    Reset => Reset,
```

```
    D_out0 => R0,
```

```
    D_out1 => R1,
```

```
    D_out2 => R2,
```

```
    D_out3 => R3,
```

```
    D_out4 => R4,
```

```
    D_out5 => R5,
```

```
    D_out6 => R6,
```

```
    D_out7 => R7
```

```
);
```

```

LED0 <= R7(0);
LED1 <= R7(1);
LED2 <= R7(2);
LED3 <= R7(3);

Anode <= "1110";
S_7Seg <= S_7s;

end Behavioral;

```

## Simulation Files

### 4-bit Add/Sub Unit

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Add_Sub_4bit_Sim is
-- Port ( );
end Add_Sub_4bit_Sim;

architecture Behavioral of Add_Sub_4bit_Sim is

-- Component Declaration for the Unit Under Test (UUT)
component Add_Sub_4bit
    Port (
        A : in STD_LOGIC_VECTOR(3 downto 0);
        B : in STD_LOGIC_VECTOR(3 downto 0);
        AddSubSelect : in STD_LOGIC;
        S : inout STD_LOGIC_VECTOR(3 downto 0);
        Zero : out STD_LOGIC;
        Overflow : out STD_LOGIC
    );
end component;

-- Signals for testbench
signal A : STD_LOGIC_VECTOR(3 downto 0);
signal B : STD_LOGIC_VECTOR(3 downto 0);
signal AddSubSelect : STD_LOGIC;
signal S : STD_LOGIC_VECTOR(3 downto 0);
signal Zero : STD_LOGIC;
signal Overflow : STD_LOGIC;

```

```
begin
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: Add_Sub_4bit
```

```
  Port Map (
```

```
    A => A,
```

```
    B => B,
```

```
    AddSubSelect => AddSubSelect,
```

```
    S => S,
```

```
    Zero => Zero,
```

```
    Overflow => Overflow
```

```
  );
```

```
-- Stimulus Process
```

```
stim_proc: process
```

```
begin
```

```
  -- Test 1: for index 230111X
```

```
  A <= "1111";
```

```
  B <= "1101";
```

```
  AddSubSelect <= '0'; -- Addition
```

```
  wait for 100 ns;
```

```
  A <= "1111";
```

```
  B <= "1101";
```

```
  AddSubSelect <= '1'; -- Subtraction
```

```
  wait for 100 ns;
```

```
  -- Test 2: for index 230315C
```

```
  A <= "1011";
```

```
  B <= "1010";
```

```
  AddSubSelect <= '0'; -- Addition
```

```
  wait for 100 ns;
```

```
  A <= "1011";
```

```
  B <= "1010";
```

```
  AddSubSelect <= '1'; -- Subtraction
```

```
  wait for 100 ns;
```

```
  -- Test 3: for index 230501T
```

```
  A <= "0101";
```

```
  B <= "0110";
```

```
  AddSubSelect <= '0'; -- Addition
```

```
  wait for 100 ns;
```

```
  A <= "0101";
```



```

    B <= "0110";
    AddSubSelect <= '1'; -- Subtraction
    wait for 100 ns;

    -- Test 2: for index 230571F
    A <= "1011";
    B <= "1010";
    AddSubSelect <= '0'; -- Addition
    wait for 100 ns;

    A <= "1011";
    B <= "1010";
    AddSubSelect <= '1'; -- Subtraction
    wait for 100 ns;

    -- End simulation
    wait;
end process;

end Behavioral;

```

3-bit Program Counter

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity PC_3bit_Sim is
end PC_3bit_Sim;

architecture Behavioral of PC_3bit_Sim is
    -- Component Declaration for the Unit Under Test (UUT)
    component PC_3bit
        Port (
            Reset          : in STD_LOGIC;
            Clk            : in STD_LOGIC;
            MemorySelect   : out STD_LOGIC_VECTOR (2 downto 0);
            JumpAddr       : in STD_LOGIC_VECTOR (2 downto 0);
            JumpFlag       : in STD_LOGIC
        );
    end component;

    -- Inputs
    signal Reset : STD_LOGIC := '0';
    signal Clk   : STD_LOGIC := '0';

```

```

signal JumpAddr : STD_LOGIC_VECTOR(2 downto 0) := "000";
signal JumpFlag : STD_LOGIC := '0';

-- Outputs
signal MemorySelect : STD_LOGIC_VECTOR(2 downto 0);

-- Clock period definitions
constant Clk_period : time := 100 ns;

begin
  -- Instantiate the Unit Under Test (UUT)
  uut: PC_3bit port map (
    Reset => Reset,
    Clk => Clk,
    MemorySelect => MemorySelect,
    JumpAddr => JumpAddr,
    JumpFlag => JumpFlag
  );

  -- Clock process definitions
  Clk_process: process
  begin
    Clk <= '0';
    wait for Clk_period/2;
    Clk <= '1';
    wait for Clk_period/2;
  end process;

  -- Stimulus process
  stim_proc: process
  begin
    -- Phase 1: Initial Reset
    Reset <= '1';
    wait for Clk_period*2;
    Reset <= '0';

    -- Phase 2: Count normally for 3 cycles (expect 001,
010, 011)
    wait for Clk_period*3;

    -- Phase 3: Jump to 5 ("101")
    JumpAddr <= "101";
    JumpFlag <= '1';
    wait for Clk_period;
    JumpFlag <= '0';
  end process;
end;

```

```

        Reset <= '0';
        -- Phase 4: Count normally for 1 cycle (expect 110)
        wait for Clk_period*3;

        -- End simulation
        wait;
    end process;
end Behavioral;

```

#### Program Rom

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Program_ROM_Sim is
-- Port ( );
end Program_ROM_Sim;

architecture Behavioral of Program_ROM_Sim is

    -- Component declaration of Program_ROM
    component Program_ROM
        Port (
            MemSelect : in STD_LOGIC_VECTOR(2 downto 0);
            InstructBus : out STD_LOGIC_VECTOR(11 downto 0)
        );
    end component;

    -- Testbench signals
    signal MemSelect      : STD_LOGIC_VECTOR(2 downto 0);
    signal InstructBus    : STD_LOGIC_VECTOR(11 downto 0);

begin

    -- Instantiate the Program_ROM
    uut: Program_ROM
        port map (
            MemSelect    => MemSelect,
            InstructBus  => InstructBus
        );

    -- Test process to simulate ROM output
    stim_proc: process
    begin
        -- Loop through all addresses from 0 to 7
    end process;
end Behavioral;

```

```

        for i in 0 to 7 loop
            MemSelect <= std_logic_vector(to_unsigned(i, 3));
            wait for 100 ns; -- Wait for propagation
        end loop;

        -- Finish simulation
        wait;
    end process;

end Behavioral;

```

### Register Bank

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Register_Bank_Sim is
    -- Port ( );
end Register_Bank_Sim;

architecture Behavioral of Register_Bank_Sim is

    component Register_Bank
        Port (
            D_input : in STD_LOGIC_VECTOR (3 downto 0);
            Reg_En : in STD_LOGIC_VECTOR (2 downto 0);
            Clock : in STD_LOGIC;
            Reset : in STD_LOGIC;
            D_out0 : out STD_LOGIC_VECTOR (3 downto 0);
            D_out1 : out STD_LOGIC_VECTOR (3 downto 0);
            D_out2 : out STD_LOGIC_VECTOR (3 downto 0);
            D_out3 : out STD_LOGIC_VECTOR (3 downto 0);
            D_out4 : out STD_LOGIC_VECTOR (3 downto 0);
            D_out5 : out STD_LOGIC_VECTOR (3 downto 0);
            D_out6 : out STD_LOGIC_VECTOR (3 downto 0);
            D_out7 : out STD_LOGIC_VECTOR (3 downto 0)
        );
    end component;

    -- Signals
    signal D_input : STD_LOGIC_VECTOR(3 downto 0);
    signal Reg_En : STD_LOGIC_VECTOR(2 downto 0);
    signal Clock : STD_LOGIC := '0';

```

```

    signal Reset    : STD_LOGIC;

    signal D_out0, D_out1, D_out2, D_out3,
           D_out4, D_out5, D_out6, D_out7 : STD_LOGIC_VECTOR(3
downto 0);

    -- Clock process
    constant clk_period : time := 100 ns;
begin

    -- Clock generator
    clk_process : process
    begin
        while true loop
            Clock <= '0';
            wait for clk_period / 2;
            Clock <= '1';
            wait for clk_period / 2;
        end loop;
    end process;

    -- Instantiate the Unit Under Test (UUT)
    uut: Register_Bank
        port map (
            D_input => D_input,
            Reg_En => Reg_En,
            Clock => Clock,
            Reset => Reset,
            D_out0 => D_out0,
            D_out1 => D_out1,
            D_out2 => D_out2,
            D_out3 => D_out3,
            D_out4 => D_out4,
            D_out5 => D_out5,
            D_out6 => D_out6,
            D_out7 => D_out7
        );

    -- Stimulus
    stim_proc : process
    begin
        -- Initial values
        Reset <= '1';
        D_input <= "0000";
        Reg_En <= "000";
        wait for clk_period;

```

```

-- Release reset
Reset <= '0';
wait for clk_period;
-- Test 1: For index 230111X
D_input <= "1111";
Reg_En <= "001";
wait for clk_period;

D_input <= "1101";
Reg_En <= "010";
wait for clk_period;

-- Test 2: For index 230315C and 230571F
D_input <= "1011";
Reg_En <= "011";
wait for clk_period;

D_input <= "1010";
Reg_En <= "100";
wait for clk_period;

-- Test 3: For index 230501T
D_input <= "0101";
Reg_En <= "101";
wait for clk_period;

D_input <= "0110";
Reg_En <= "110";
wait for clk_period;
-- Wait and then reset everything
wait for 4 * clk_period;
Reset <= '1';
wait for clk_period;

-- Release reset
Reset <= '0';
wait;

end process;

end Behavioral;

```

Register

```

library IEEE;

```

```

use IEEE.STD_LOGIC_1164.ALL;

entity TB_Reg is
end TB_Reg;

architecture Behavioral of TB_Reg is

    -- Component Declaration for the Unit Under Test (UUT)
    component Reg
        Port (
            D      : in  STD_LOGIC_VECTOR(3 downto 0);
            En     : in  STD_LOGIC;
            Clk    : in  STD_LOGIC;
            Reset  : in  STD_LOGIC;
            Q      : out STD_LOGIC_VECTOR(3 downto 0)
        );
    end component;

    -- Testbench signals
    signal D_tb      : STD_LOGIC_VECTOR(3 downto 0) := (others =>
'0');
    signal En_tb     : STD_LOGIC := '0';
    signal Clk_tb    : STD_LOGIC := '0';
    signal Reset_tb  : STD_LOGIC := '0';
    signal Q_tb      : STD_LOGIC_VECTOR(3 downto 0);

    -- Clock generation process (10 ns period)
    constant clk_period : time := 100 ns;

begin

    -- Instantiate the Unit Under Test (UUT)
    UUT: Reg
        port map (
            D      => D_tb,
            En     => En_tb,
            Clk    => Clk_tb,
            Reset  => Reset_tb,
            Q      => Q_tb
        );

    -- Clock process
    clk_process: process
    begin
        while true loop
            Clk_tb <= '0';

```

```
        wait for clk_period / 2;
        Clk_tb <= '1';
        wait for clk_period / 2;
    end loop;
end process;

-- Stimulus process
stim_proc: process
begin
    -- Reset the register
    Reset_tb <= '1';
    wait for clk_period;
    Reset_tb <= '0';

    -- Test 1: For index 230111X
    D_tb <= "1111";
    En_tb <= '1';
    wait for clk_period;

    -- Change D to 1101, but En=0 (Q should remain 1111)
    D_tb <= "1101";
    En_tb <= '0';
    wait for clk_period;

    -- Enable again, Q should update to 1101
    En_tb <= '1';
    wait for clk_period;

    -- Test 2: For index 230315C and 230571F
    D_tb <= "1011";
    En_tb <= '1';
    wait for clk_period;

    -- Change D to 1010, but En=0 (Q should remain 1011)
    D_tb <= "1010";
    En_tb <= '0';
    wait for clk_period;

    -- Enable again, Q should update to 1010
    En_tb <= '1';
    wait for clk_period;

    -- Test 3: For index 230501T
    D_tb <= "0101";
    En_tb <= '1';
    wait for clk_period;
```



```

        -- Change D to 0110, but En=0 (Q should remain 0101)
        D_tb <= "0110";
        En_tb <= '0';
        wait for clk_period;

        -- Enable again, Q should update to 0110
        En_tb <= '1';
        wait for clk_period;
        -- Reset again
        Reset_tb <= '1';
        wait for clk_period;
        Reset_tb <= '0';

        wait;
    end process;

end Behavioral;

```

#### Decoder 3 to 8

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity TB_Decoder_3_to_8 is
end TB_Decoder_3_to_8;

architecture Behavioral of TB_Decoder_3_to_8 is

    -- Component Declaration for Unit Under Test (UUT)
    component Decoder_3_to_8
        Port (
            I : in STD_LOGIC_VECTOR (2 downto 0);
            EN : in STD_LOGIC;
            Y : out STD_LOGIC_VECTOR (7 downto 0)
        );
    end component;

    -- Testbench signals
    signal I_tb  : STD_LOGIC_VECTOR(2 downto 0) := (others =>
'0');
    signal EN_tb : STD_LOGIC := '0';
    signal Y_tb  : STD_LOGIC_VECTOR(7 downto 0);

```

```

begin

    -- Instantiate the Unit Under Test (UUT)
    UUT: Decoder_3_to_8
        port map (
            I  => I_tb,
            EN => EN_tb,
            Y  => Y_tb
        );

    -- Stimulus process
    stim_proc: process
    begin
        -- Test all inputs with Enable = '0' (Y should be
00000000)
        EN_tb <= '0';
        for i in 0 to 7 loop
            I_tb <= std_logic_vector(to_unsigned(i, 3));
            wait for 50 ns;
        end loop;

        -- Enable the decoder and test all input combinations
        EN_tb <= '1';
        for i in 0 to 7 loop
            I_tb <= std_logic_vector(to_unsigned(i, 3));
            wait for 50 ns;
        end loop;

        wait;
    end process;

end Behavioral;

```

#### LUT\_16\_7

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

entity LUT_16_7 is
    Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
          data : out STD_LOGIC_VECTOR (6 downto 0));
end LUT_16_7;

architecture Behavioral of LUT_16_7 is

```

```

type rom_type is array (0 to 15) of std_logic_vector(6 downto 0);
signal sevenSegment_ROM : rom_type := (
    "1000000", -- 0      0= on 1=off    g f e d c b a
    "1111001", -- 1
    "0100100", -- 2
    "0110000", -- 3
    "0011001", -- 4
    "0010010", -- 5
    "0000010", -- 6
    "1111000", -- 7
    "0000000", -- 8
    "0010000", -- 9
    "0001000", -- a
    "0000011", -- b
    "1000110", -- c
    "0100001", -- d
    "0000110", -- e
    "0001110"  -- f
);

```

```

begin
    data <= sevenSegment_ROM(to_integer(unsigned(address)));

end Behavioral;

```

#### Slow Clock

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_Slow_Clk is
-- Testbench has no ports
end TB_Slow_Clk;

architecture Behavioral of TB_Slow_Clk is

    -- Component declaration of the Unit Under Test (UUT)
    component Slow_Clk
        Port (
            Clk_in : in STD_LOGIC;
            Clk_out : out STD_LOGIC
        );
    end component;

```

```

-- Testbench signals
signal Clk_in_tb : STD_LOGIC := '0';
signal Clk_out_tb : STD_LOGIC;

constant clk_period : time := 10 ns; -- Simulated clock period

begin

-- Instantiate the Unit Under Test (UUT)
 uut: Slow_Clk
   Port map (
     Clk_in => Clk_in_tb,
     Clk_out => Clk_out_tb
   );

-- Clock generation process
 clk_process : process
 begin
   while now < 500 ns loop -- run for limited simulation
time
       Clk_in_tb <= '0';
       wait for clk_period / 2;
       Clk_in_tb <= '1';
       wait for clk_period / 2;
   end loop;
   wait; -- stop simulation
 end process;

end Behavioral;

```

#### MUX 2way 4bit

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_Mux_2way_4bit is
-- no ports for testbench
end TB_Mux_2way_4bit;

architecture Behavioral of TB_Mux_2way_4bit is

-- Component declaration
component Mux_2way_4bit
  Port ( AddSub : in STD_LOGIC_VECTOR (3 downto 0);
        Immediate_Val : in STD_LOGIC_VECTOR (3 downto 0);
        Load_Select : in STD_LOGIC;

```

```

        output : out STD_LOGIC_VECTOR (3 downto 0));
end component;

-- Test signals
signal AddSub_tb : STD_LOGIC_VECTOR(3 downto 0) := (others =>
'0');
signal Immediate_Val_tb : STD_LOGIC_VECTOR(3 downto 0) :=
(others => '0');
signal Load_Select_tb : STD_LOGIC := '0';
signal output_tb : STD_LOGIC_VECTOR(3 downto 0);

begin

-- Instantiate the Unit Under Test (UUT)
UUT: Mux_2way_4bit port map(
    AddSub => AddSub_tb,
    Immediate_Val => Immediate_Val_tb,
    Load_Select => Load_Select_tb,
    output => output_tb
);

-- Stimulus process
stim_proc: process
begin
    -- Test case 1: for index 230111X Load_Select = 0, select
Immediate_Val
    Immediate_Val_tb <= "1111";
    AddSub_tb <= "1101";
    Load_Select_tb <= '0';
    wait for 100 ns;

    Load_Select_tb <= '1';
    wait for 100 ns;

    -- Test case 2: for index 230315C Load_Select = 0, select
Immediate_Val
    Immediate_Val_tb <= "1011";
    AddSub_tb <= "1010";
    Load_Select_tb <= '0';
    wait for 100 ns;

    Load_Select_tb <= '1';
    wait for 100 ns;

    -- Test case 3: for index 230501T Load_Select = 0, select
Immediate_Val

```

```

        Immediate_Val_tb <= "0101";
        AddSub_tb <= "0110";
        Load_Select_tb <= '0';
        wait for 100 ns;

        Load_Select_tb <= '1';
        wait for 100 ns;

        -- Test case 4: for index 230571F Load_Select = 0, select
Immediate_Val
        Immediate_Val_tb <= "1011";
        AddSub_tb <= "1010";
        Load_Select_tb <= '0';
        wait for 100 ns;

        Load_Select_tb <= '1';
        wait for 100 ns;
        -- Finish simulation
        wait;
    end process;

end Behavioral;

```

#### MUX 8way 4bit

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity TB_Mux_8way_4bit is
end TB_Mux_8way_4bit;

architecture Behavioral of TB_Mux_8way_4bit is

    component Mux_8way_4bit
        Port (
            reg0 : in STD_LOGIC_VECTOR (3 downto 0);
            reg1 : in STD_LOGIC_VECTOR (3 downto 0);
            reg2 : in STD_LOGIC_VECTOR (3 downto 0);
            reg3 : in STD_LOGIC_VECTOR (3 downto 0);
            reg4 : in STD_LOGIC_VECTOR (3 downto 0);
            reg5 : in STD_LOGIC_VECTOR (3 downto 0);
            reg6 : in STD_LOGIC_VECTOR (3 downto 0);
            reg7 : in STD_LOGIC_VECTOR (3 downto 0);
            Reg_select : in STD_LOGIC_VECTOR (2 downto 0);
            output : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

```

```

    signal reg0_tb, reg1_tb, reg2_tb, reg3_tb, reg4_tb, reg5_tb,
    reg6_tb, reg7_tb : STD_LOGIC_VECTOR(3 downto 0);
    signal Reg_select_tb : STD_LOGIC_VECTOR(2 downto 0);
    signal output_tb : STD_LOGIC_VECTOR(3 downto 0);

begin

    UUT: Mux_8way_4bit
        port map(
            reg0 => reg0_tb,
            reg1 => reg1_tb,
            reg2 => reg2_tb,
            reg3 => reg3_tb,
            reg4 => reg4_tb,
            reg5 => reg5_tb,
            reg6 => reg6_tb,
            reg7 => reg7_tb,
            Reg_select => Reg_select_tb,
            output => output_tb
        );

    stim_proc: process
    begin
        -- Initialize all inputs
        -- index 230111X
        reg0_tb <= "1111";
        reg1_tb <= "1101";
        -- index 230315C
        reg2_tb <= "1011";
        reg3_tb <= "1010";
        -- index 230501T
        reg4_tb <= "0101";
        reg5_tb <= "0110";
        -- index 230571F
        reg6_tb <= "1011";
        reg7_tb <= "1010";

        -- Test all select lines
        for i in 0 to 7 loop
            Reg_select_tb <= std_logic_vector(to_unsigned(i, 3));
            wait for 100 ns;
        end loop;

        wait;
    end process;

```

```
end Behavioral;
```

### Instruction Decoder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_Instruction_Decoder is
end TB_Instruction_Decoder;

architecture Behavioral of TB_Instruction_Decoder is

    -- Component Declaration
    component Instruction_Dec
        Port (
            Reg_En          : out STD_LOGIC_VECTOR (2 downto 0);
            Load_Select     : out STD_LOGIC;
            Immediate_Val   : out STD_LOGIC_VECTOR (3 downto 0);
            MuxA_Select     : out STD_LOGIC_VECTOR (2 downto 0);
            MuxB_Select     : out STD_LOGIC_VECTOR (2 downto 0);
            AddSub_Select   : out STD_LOGIC;
            JmpFlag         : out STD_LOGIC;
            JmpAddr         : out STD_LOGIC_VECTOR (2 downto 0);
            Instruct_Bus    : in  STD_LOGIC_VECTOR (11 downto 0);
            JumpCheck       : in  STD_LOGIC_VECTOR (3 downto 0)
        );
    end component;

    -- Signals
    signal Reg_En          : STD_LOGIC_VECTOR (2 downto 0);
    signal Load_Select     : STD_LOGIC;
    signal Immediate_Val   : STD_LOGIC_VECTOR (3 downto 0);
    signal MuxA_Select     : STD_LOGIC_VECTOR (2 downto 0);
    signal MuxB_Select     : STD_LOGIC_VECTOR (2 downto 0);
    signal AddSub_Select   : STD_LOGIC;
    signal JmpFlag         : STD_LOGIC;
    signal JmpAddr         : STD_LOGIC_VECTOR (2 downto 0);
    signal Instruct_Bus    : STD_LOGIC_VECTOR (11 downto 0);
    signal JumpCheck       : STD_LOGIC_VECTOR (3 downto 0);

begin

    -- Instantiate the Unit Under Test (UUT)
    uut: Instruction_Dec
        Port Map (
```



```

        Reg_En      => Reg_En,
        Load_Select => Load_Select,
        Immediate_Val => Immediate_Val,
        MuxA_Select  => MuxA_Select,
        MuxB_Select  => MuxB_Select,
        AddSub_Select => AddSub_Select,
        JmpFlag      => JmpFlag,
        JmpAddr      => JmpAddr,
        Instruct_Bus => Instruct_Bus,
        JumpCheck    => JumpCheck
    );

-- Stimulus Process
stim_proc: process
begin
    -- Test ADD (opcode "00"), A=001, B=010
    Instruct_Bus <= "00" & "001" & "010" & "0000"; -- 2 + 3 +
3 + 4 = 12 bits
    JumpCheck <= "0000";
    wait for 100 ns;

    -- Test NEG (opcode "01"), B=011
    Instruct_Bus <= "01" & "011" & "000" & "0000"; -- A =
unused here
    wait for 100 ns;

    -- Test MOV (opcode "10"), Reg=100, Imm=1100
    Instruct_Bus <= "10" & "100" & "000" & "1100";
    wait for 100 ns;

    -- Test JMP with JumpCheck = 0000 (should jump), A=101,
Addr=011
    Instruct_Bus <= "11" & "101" & "000" & "0011";
    JumpCheck <= "0000";
    wait for 100 ns;

    -- Test JMP with JumpCheck ? 0000 (no jump), A=110,
Addr=101
    Instruct_Bus <= "11" & "110" & "000" & "0101";
    JumpCheck <= "1111";
    wait for 100 ns;

    wait;
end process;

end Behavioral;
```

## Nano Processor

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_TEXTIO.all; -- For hwwrite
use STD.TEXTIO.all;           -- For file operations

entity TB_Nanoprocessor is
end TB_Nanoprocessor;

architecture Behavioral of TB_Nanoprocessor is

    component Nanoprocessor is
        Port (
            Reset : in STD_LOGIC;
            clk : in STD_LOGIC;
            Zero_LED : out STD_LOGIC;
            Overflow_LED : out STD_LOGIC;
            LED0 : out STD_LOGIC;
            LED1 : out STD_LOGIC;
            LED2 : out STD_LOGIC;
            LED3 : out STD_LOGIC;
            Anode : out STD_LOGIC_VECTOR (3 downto 0);
            S_7Seg : out STD_LOGIC_VECTOR (6 downto 0)
        );
    end component;

    -- Signals
    signal clk          : STD_LOGIC := '0';
    signal reset        : STD_LOGIC := '1';
    signal zero_led     : STD_LOGIC;
    signal overflow_led : STD_LOGIC;
    signal led0, led1, led2, led3 : STD_LOGIC;
    signal anode        : STD_LOGIC_VECTOR(3 downto 0);
    signal s_7seg       : STD_LOGIC_VECTOR(6 downto 0);

    -- Clock period
    constant clk_period : time := 10 ns;

    -- Simulation control
    signal sim_finished : boolean := false;

    -- Function to convert std_logic_vector to string
    function vec2str(vec: std_logic_vector) return string is

```

```

        variable result: string(1 to vec'length);
begin
    for i in vec'range loop
        result(i+1) := std_logic'image(vec(i))(2);
    end loop;
    return result;
end function;

begin

-- Instantiate Unit Under Test
 uut: Nanoprocessor
port map (
    Reset => reset,
    clk => clk,
    Zero_LED => zero_led,
    Overflow_LED => overflow_led,
    LED0 => led0,
    LED1 => led1,
    LED2 => led2,
    LED3 => led3,
    Anode => anode,
    S_7Seg => s_7seg
);

-- Clock generation
clk_process: process
begin
    while not sim_finished loop
        clk <= '0';
        wait for clk_period/2;
        clk <= '1';
        wait for clk_period/2;
    end loop;
    wait;
end process;

-- Stimulus process
stim_proc: process
begin
    -- Initial reset
    reset <= '1';
    wait for 20 ns;
    reset <= '0';

    -- Allow enough time for all 8 instructions to execute

```

```

    wait for 80 * clk_period;

    wait for 10 ns;

    reset <= '1';
    wait for 20 ns;
    reset <= '0';

    wait for 80 * clk_period;
    -- Check final outputs
    wait for 10 ns;


    wait;
end process;

end Behavioral;

```

## Timing Diagrams


### 4-bit Add/Sub Unit

 


## 3-bit Program Counter




## Program Rom

 


## Register Bank

 


## Register

 


## Decoder 3 to 8

 


## LUT\_16\_7

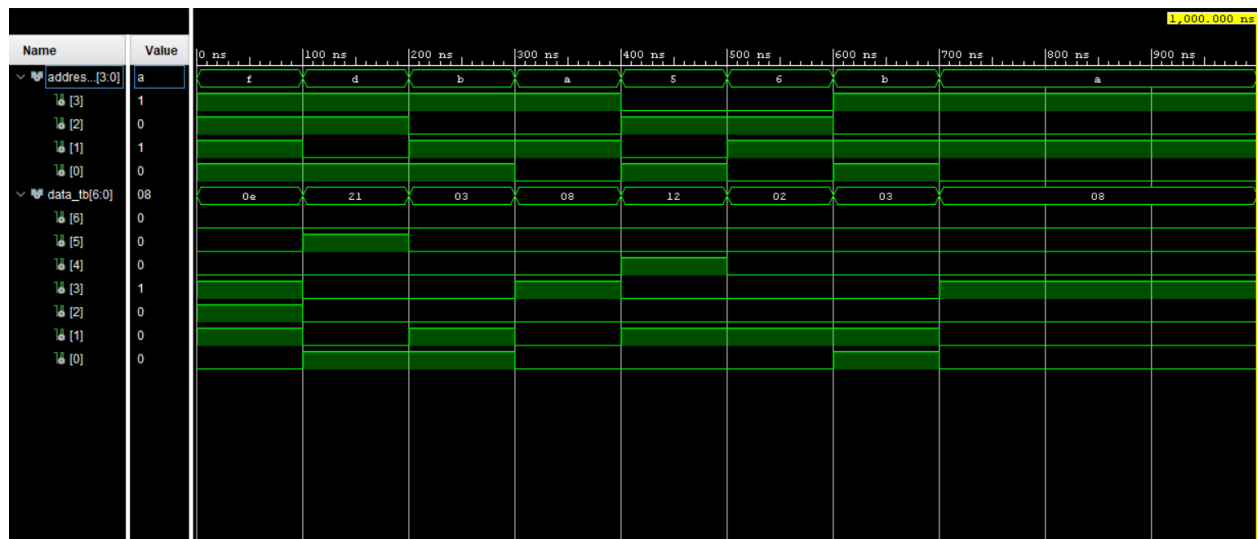

## Slow Clock

 


## MUX 2way 4bit

 





## MUX 8way 4bit

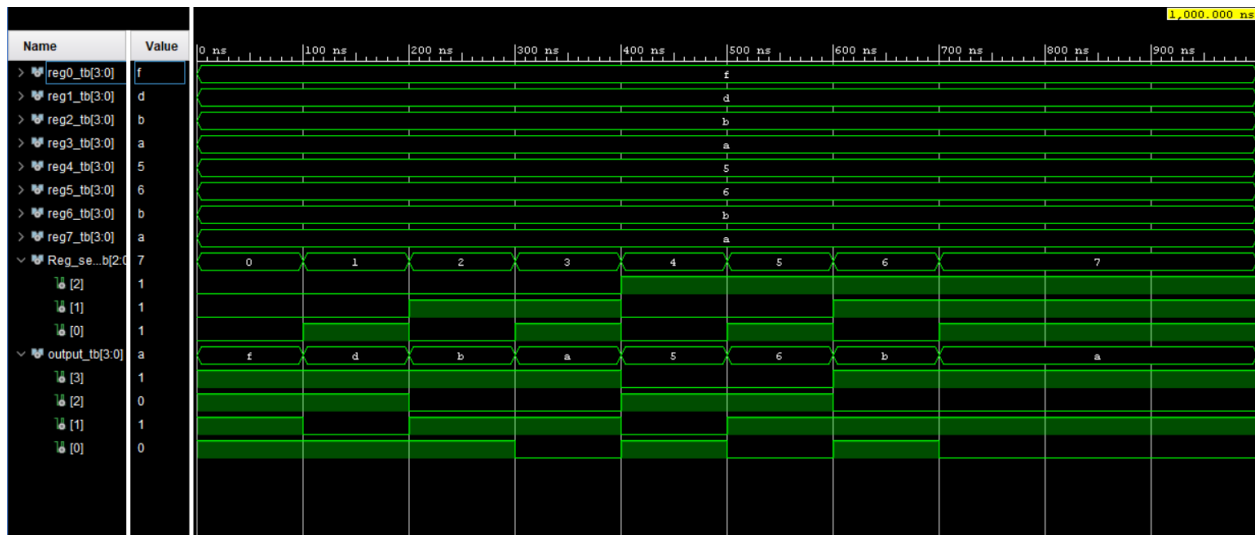

## Instruction decoder

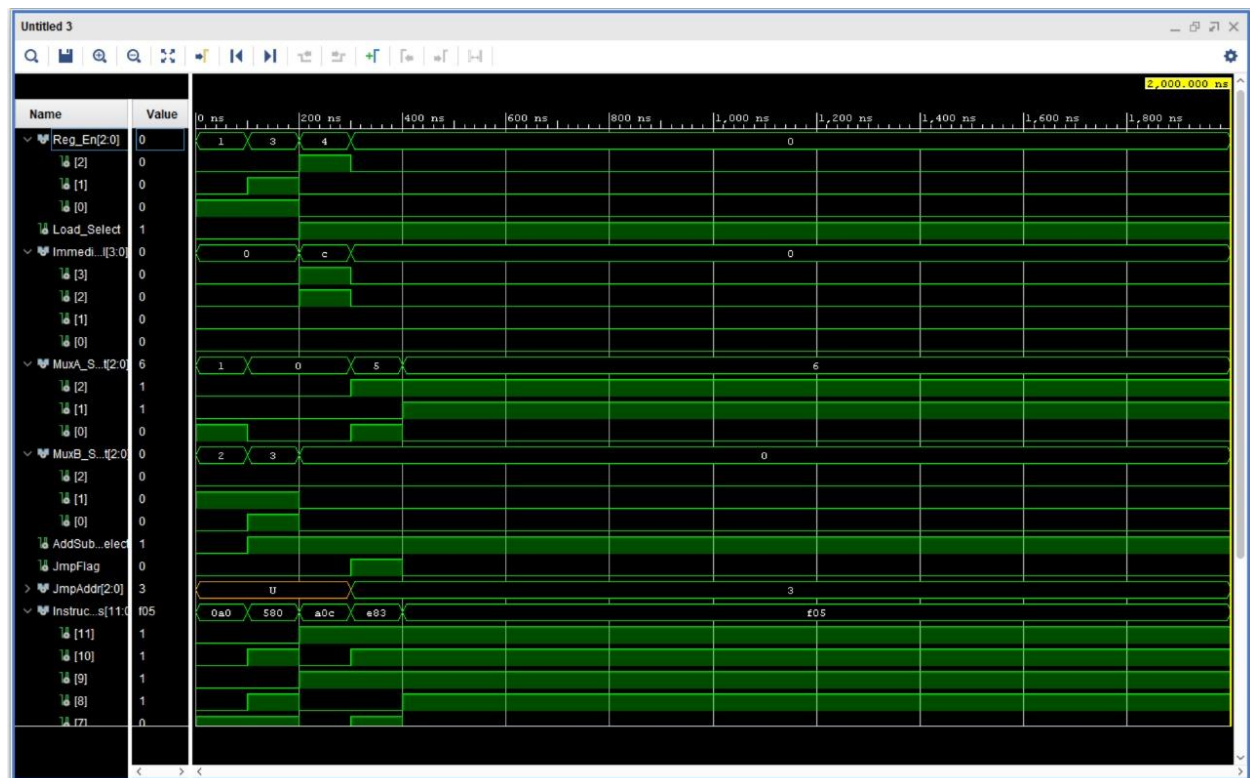

## Nano processor

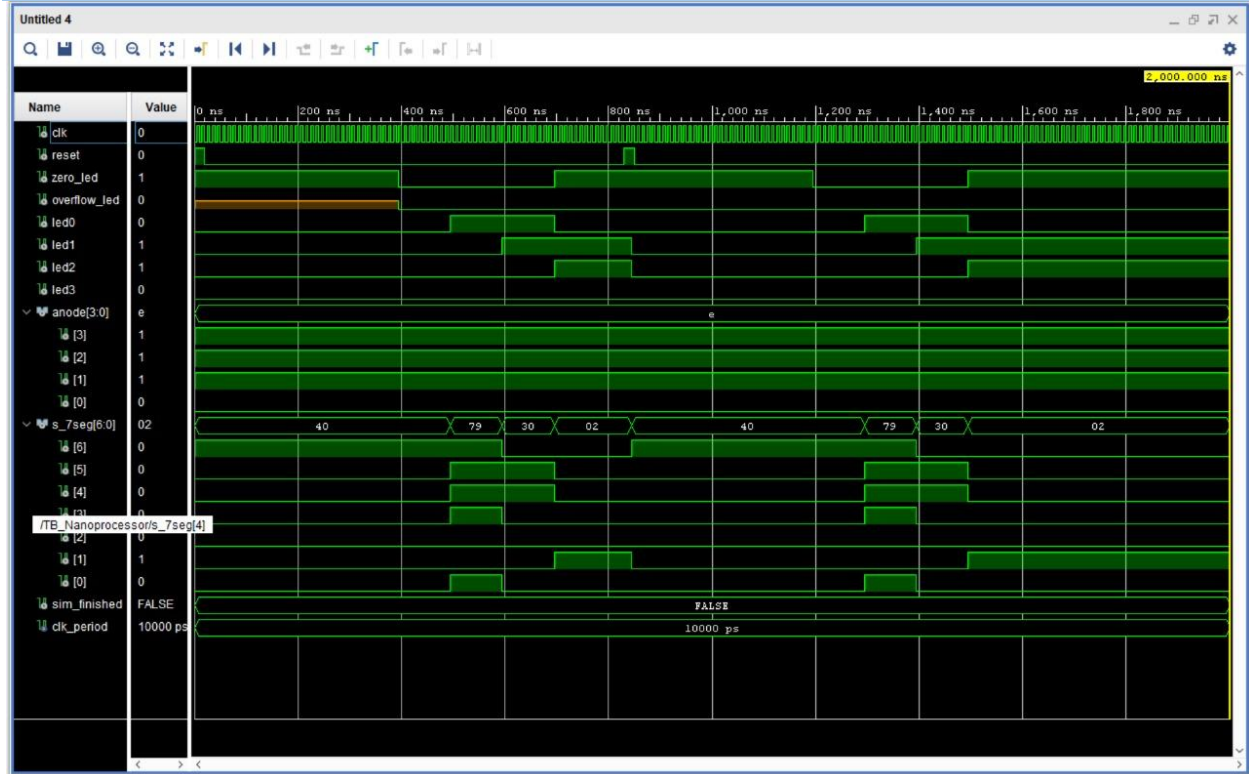

## Resource Utilization

Name	Slice LUTs (20800)	Slice Registers (41600)	Slice (8150)	LUT as Logic (20800)	LUT Flip Flop Pairs (20800)	Bonded IOB (106)	BUFGCTRL (32)
<b>Nanoprocessor</b>	29	28	11	29	9	19	1
Instruction_Decoder (I...	0	5	2	0	0	0	0
Programming_Count...	19	3	6	19	3	0	0
<b>RegisterBank (Registe...</b>	9	16	6	9	0	0	0
Reg1 (Reg)	0	4	1	0	0	0	0
Reg2 (Reg_0)	0	4	1	0	0	0	0
Reg3 (Reg_1)	5	4	3	5	0	0	0
Reg7 (Reg_2)	4	4	3	4	0	0	0
Slow_Clock (Slow_Clk)	2	4	1	2	2	0	0

## Issues and Solutions

### Program Counter (PC\_3bit) Synchronization Problem [Fixed]

#### Issue Identified:

- The original implementation using separate components (Mux\_2way\_3bit + RCA\_3 adder) caused timing violations when The JumpFlag signal arrived later than the clock edge.

#### Possible Root Causes:

- Component Propagation Delays from the 3-bit ripple-carry adder (RCA\_3) and the multiplexer.
- The JumpFlag control signal could change too close to the clock edge causing non-deterministic behavior.

#### Solution Implemented:

- Removed the 3-bit ripple-carry adder (RCA\_3) and the multiplexer which were causing the delays and replaced with case based incrementor and inline jump logic.

### Zero Flag and LED Synchronization Issue [Fix not implemented]

#### Issue Identified:

- There is a consistent 50ns delay between the zero-flag activation and the corresponding LED outputs turning off.

#### Possible Root Causes:

- The zero flag was generated combinatorially from ALU outputs. This maybe creating a critical path that must be resolved before LEDs update.

#### Proposed Solution:

- Adding a synchronized flag register that updates with the ALU result and using the registered zero flag (not combinational) to drive the zero LED.

## Conclusions

- Through this lab, we successfully engineered a functional 4-bit nanoprocessor capable of executing a basic instruction set. Key accomplishments included the development of a 4-bit arithmetic unit for signed addition and subtraction, the design of a 3-bit adder for incrementing the Program Counter (PC), and the implementation of a PC using D Flip-Flops with reset capability. Additionally, we constructed k-way b-bit multiplexers for effective control and data routing, and built an Instruction Decoder to ensure precise control of processor operations by selectively activating relevant components.
- The project emphasized the importance of collaboration, with team members contributing to different subsystems in parallel. Effective communication and coordination were essential to integrate each component into a cohesive processor design.
- This lab experience offered valuable practical insight into digital circuit design and microprocessor architecture, strengthening our understanding of control logic, data path design, and collaborative engineering practices.

**Contribution of the members**

Dabarera G.D.M

- MUX 8way 4bit (Time spent: 1 day)
- MUX 2way 4bit (Time spent: 1 day)
- Lab report (Time spent: 1 day)

Kannangara T.P

- Nano processor (Time spent: 2 days)
- Instruction decoder (Time spent: 1 day)
- Slow Clock (Time spent: 1 day)

Priyadarshana D.M.R.N

- 4-bit Add/Sub Unit (Time spent: 1 day)
- Program Rom (Time spent: 1 day)
- 3-bit Adder (Time spent: 1 day)

Sampath W.I.D

- Decoder 3 to 8 (Time spent: 1 day)
- Register Bank (Time spent: 1 day)
- 3-bit Program Counter (Time spent: 1 day)

Total time spent: about 14 days